
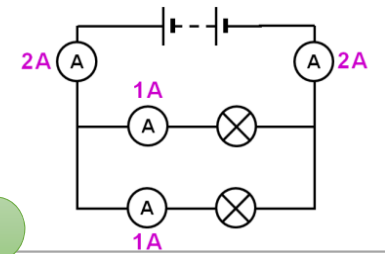
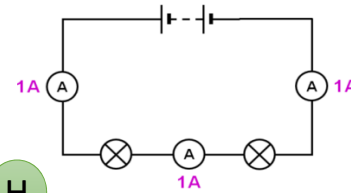


Physics Crib Sheet: Topic 2

A Current (Amps)	The flow of electric charge. The size of the current is the rate of flow of charge.
Potential Difference (Volts)	The driving force that pushes electric charge around a circuit.
Resistance (Ohms)	Anything in a circuit that reduces the flow of current.

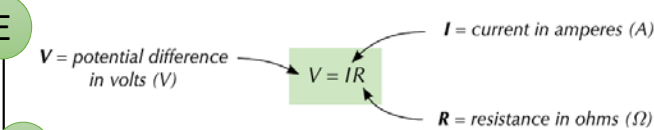


- Series circuits**
- Current is the same at all points
 - Potential difference is shared between the components.
 - Add up the pd of the components to find the pd of the power supply
 - Add up the total resistance of each component to find the total resistance of the circuit

- Parallel circuits**
- Total current in the circuit is the sum of current in each branch
 - Each branch has the same total pd as the power supply
 - Adding an extra branch containing a resistor reduces the total resistance of the circuit

B


Charge flow (C) = Current (A) x Time (s)

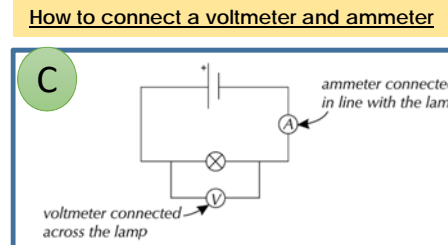- G**
- Light dependent resistors (LDR)**
- In bright light the resistance falls
 - In darkness the resistance is highest
 - Used in automatic night lights and street lamps



- Thermistors**
- When hot, the resistance drops
 - When cooler, the resistance increases
 - Used in thermostats

- J**
- Investigating the effect of wire length on current and potential difference
- 1) Attach a **crocodile clip** to the wire level with **0 cm** on the ruler.
 - 2) Attach the **second crocodile clip** to the wire a short distance from the first clip.
 - 3) Write down the **length** of the wire between the clips.
 - 4) **Close the switch**, then record the **current** through the wire and the **pd** across it.
 - 5) Use $R = V \div I$ (from the equation $V = IR$ on p.181) to **calculate the resistance** of
 - 6) **Open the switch** and **move** the second crocodile clip along the wire.
 - 7) Repeat steps 3 to 6 for a range of wire lengths.
-

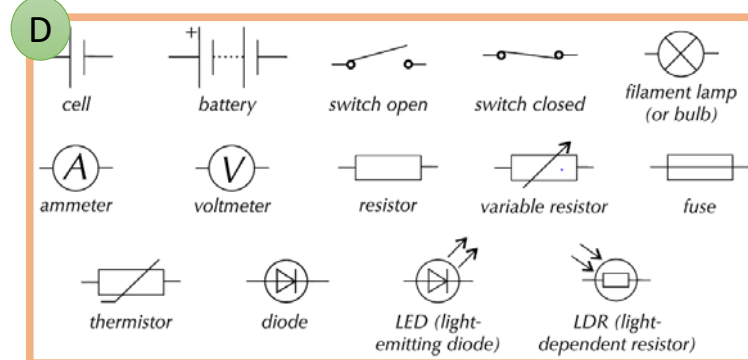

K

Energy transferred (J) = Power (W) x Time (s)

$E = QV$

$E = \text{energy transferred (J)}$

$Q = \text{charge (C)}$

$V = \text{potential difference (V)}$

